

TRAFFIC LIGHT CONTROLLER


DESIGN ASSIGNMENT #3

TRAFFIC LIGHT CONTROLLER

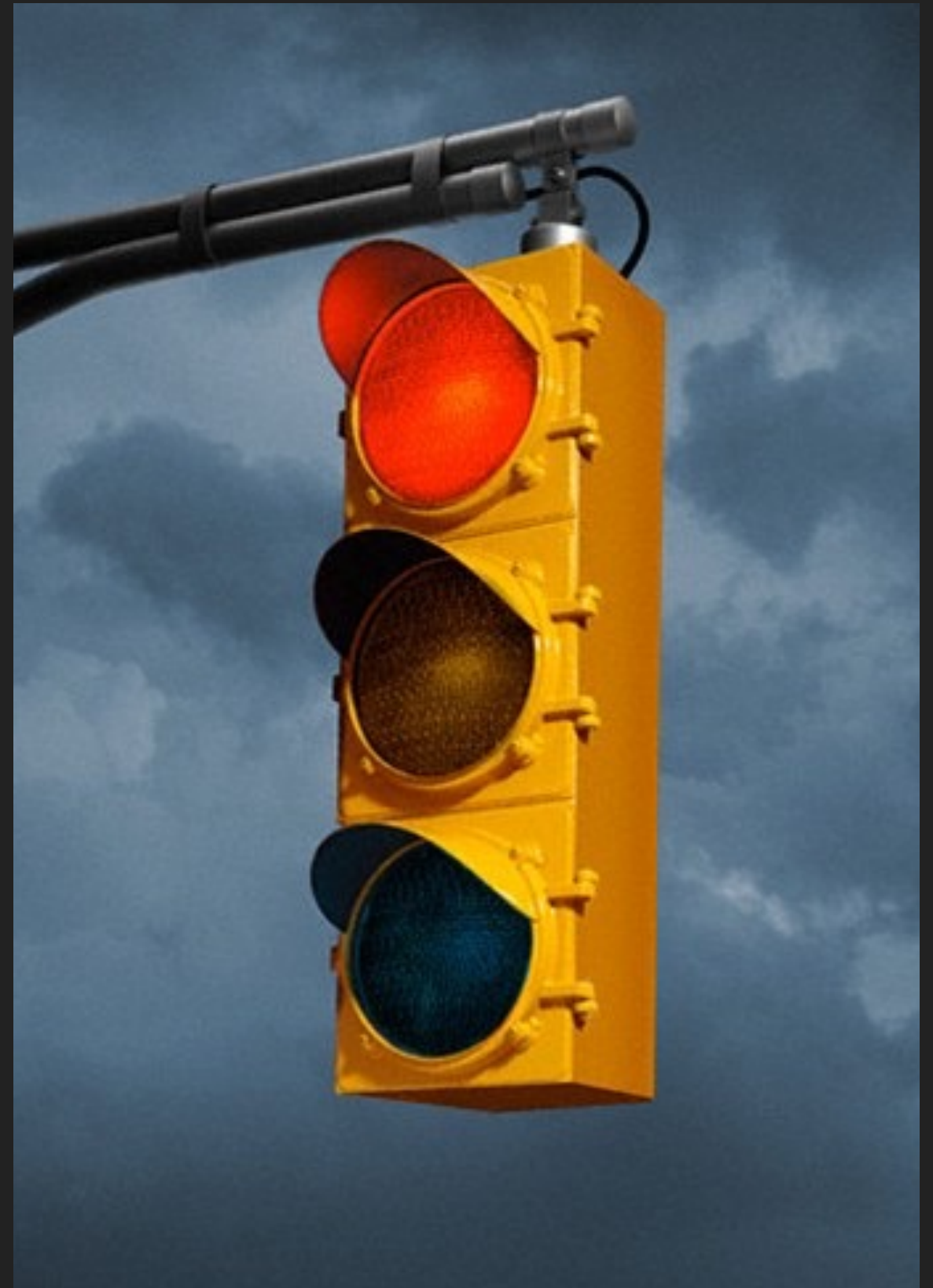PROBLEM

Design a digital controller to control traffic at an intersection of a busy main street (North-South) and an occasionally used side street (East-West).

- North South must be Green for a minimum of 25 seconds and will remain Green until traffic is present on East-West
- East West will remain Green for a maximum of 25 seconds
- Yellow lights on both streets must be for 4 seconds



SPECIFICATIONS

A blue speech bubble with a tail pointing towards the bottom-left.

TIME

A yellow speech bubble with a tail pointing towards the bottom-right.

SIGNALS

TIME SPECIFICATIONS

North-South	East-West	Both Streets
<div>32 SECONDS</div>	<div>16 SECONDS</div>	<div>4 SECONDS</div>



32 SECONDS

16 SECONDS

4 SECONDS

2^5

2^4

2^2

32 SECONDS

11111



00000

```
module nsCounter
(
    input clk,
    output [4:0] count
);

wire clk;
reg[4:0] count;

initial
    count = 0;

always @( negedge clk )
    count[0] <= ~count[0];

always @( negedge count[0] )
    count[1] <= ~count[1];

always @( negedge count[1] )
    count[2] <= ~count[2];

always @( negedge count[2] )
    count[3] <= ~count[3];

always @( negedge count[3] )
    count[4] <= ~count[4];

endmodule
```

16 SECONDS

1111



0000

```
module ewCounter
(
    input clk,
    output [3:0] count
);

wire clk;
reg[3:0] count;

initial
    count = 0;

always @( negedge clk )
    count[0] <= ~count[0];

always @( negedge count[0] )
    count[1] <= ~count[1];

always @( negedge count[1] )
    count[2] <= ~count[2];

always @( negedge count[2] )
    count[3] <= ~count[3];

endmodule
```

4 SECONDS

11



00

```
module yellowCounter
(
    input clk,
    output [1:0] count
);

wire clk;
reg[1:0] count;

initial
    count = 0;

always @( negedge clk )
    count[0] <= ~count[0];

always @( negedge count[0] )
    count[1] <= ~count[1];

endmodule
```


TIME SPECIFICATIONS


North-South	East-West	Both Streets
<div>32 SECONDS</div>	<div>16 SECONDS</div>	<div>4 SECONDS</div>

SIGNAL SPECIFICATIONS


East-West




Both Streets

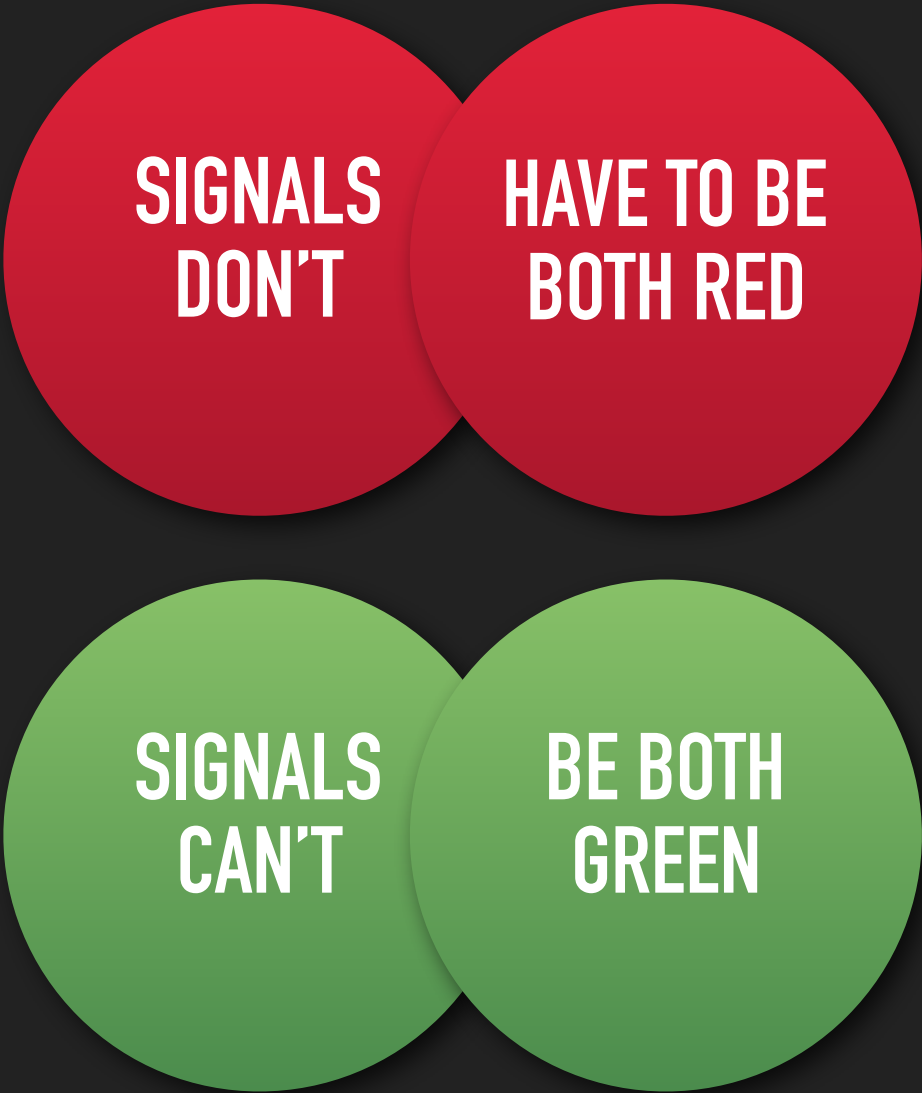

STATE BUBBLE

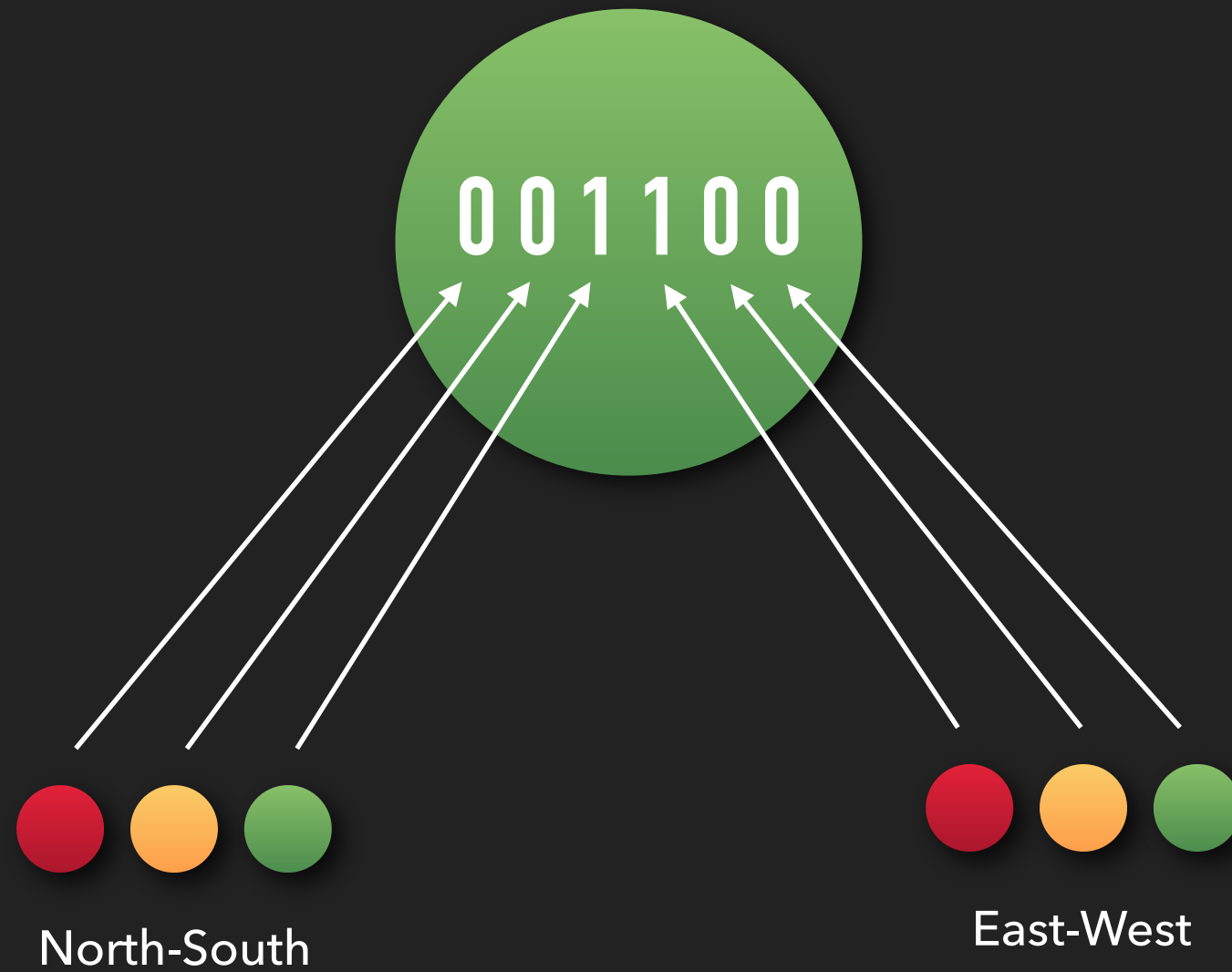

STATE DIAGRAM

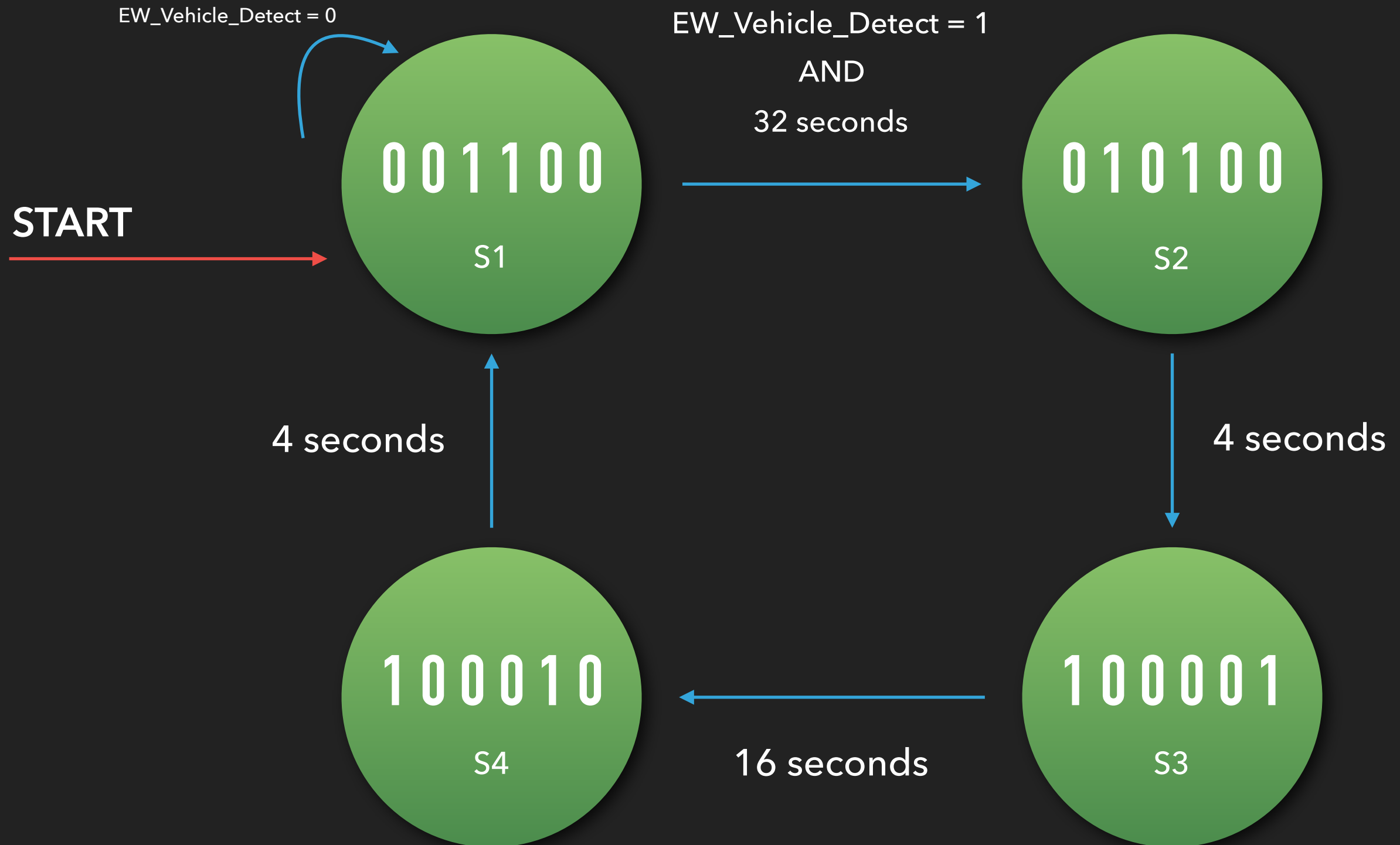

INPUTS AND OUTPUTS

Inputs (8)

NS Red

NS Yellow

NS Green

EW Red

EW Yellow

EW Green

Traffic on EW

Timer

Outputs (6)

NS Red

NS Yellow

NS Green

EW Red

EW Yellow

EW Green

TRAFFIC LIGHT CONTROLLER

TRUTH TABLE

Present State						Inputs		Future State					
NS			EW					NS			EW		
R	Y	G	R	Y	G	EW	TIME	R	Y	G	R	Y	G
0	0	1	1	0	0	0	x	0	0	1	1	0	0
0	0	1	1	0	0	1	0	0	0	1	1	0	0
0	0	1	1	0	0	1	1	0	1	0	1	0	0
0	1	0	1	0	0	x	0	0	1	0	1	0	0
0	1	0	1	0	0	x	1	1	0	0	0	0	1
1	0	0	0	0	1	x	0	1	0	0	0	0	1
1	0	0	0	0	1	x	1	1	0	0	0	1	0
1	0	0	0	1	0	x	0	1	0	1	0	1	0
1	0	0	0	1	0	x	1	0	0	1	1	0	0

TRAFFIC LIGHT CONTROLLER

K MAP OUTPUT (NORTH-SOUTH RED)

A = NS Red D = EW Red G = Traffic on EW
B = NS Yellow E = EW Yellow H = Timer
C = NS Green F = EW Green

	$\overline{E}\overline{F}\overline{G}\overline{H}$	$\overline{E}\overline{F}\overline{G}H$	$\overline{E}\overline{F}G\overline{H}$	$\overline{E}\overline{F}GH$	$\overline{E}F\overline{G}\overline{H}$	$\overline{E}F\overline{G}H$	$\overline{E}FG\overline{H}$	$\overline{E}FGH$	$E\overline{F}\overline{G}\overline{H}$	$E\overline{F}\overline{G}H$	$EFG\overline{H}$	$EFGH$	$\overline{E}\overline{F}\overline{G}\overline{H}$	$\overline{E}\overline{F}\overline{G}H$	$\overline{E}\overline{F}G\overline{H}$	$\overline{E}\overline{F}GH$
$\overline{A}\overline{B}\overline{C}\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}\overline{B}\overline{C}D$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}\overline{B}C\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}\overline{B}CD$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}B\overline{C}\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}B\overline{C}D$	0	1	1	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}BC\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}BCD$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$AB\overline{C}\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$AB\overline{C}D$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$ABC\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$ABCD$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$A\overline{B}\overline{C}\overline{D}$	0	0	0	0	1	1	1	1	0	0	0	0	1	0	0	1
$A\overline{B}\overline{C}D$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$A\overline{B}C\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$A\overline{B}CD$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0

$A'BC'DE'F'H + AB'C'DE'F + AB'C'D'EF'H' = 0101001 + 100101 + 1000100$

TRAFFIC LIGHT CONTROLLER

K MAP OUTPUT (NORTH-SOUTH YELLOW)

A = NS Red D = EW Red G = Traffic on EW
B = NS Yellow E = EW Yellow H = Timer
C = NS Green F = EW Green

	$\overline{E}\overline{F}\overline{G}\overline{H}$	$\overline{E}\overline{F}\overline{G}H$	$\overline{E}\overline{F}G\overline{H}$	$\overline{E}\overline{F}GH$	$\overline{E}F\overline{G}\overline{H}$	$\overline{E}F\overline{G}H$	$\overline{E}FG\overline{H}$	$\overline{E}FGH$	$E\overline{F}\overline{G}\overline{H}$	$E\overline{F}\overline{G}H$	$EFG\overline{H}$	$EFGH$	$\overline{E}\overline{F}\overline{G}\overline{H}$	$\overline{E}\overline{F}\overline{G}H$	$\overline{E}\overline{F}G\overline{H}$	$\overline{E}\overline{F}GH$
$\overline{A}\overline{B}\overline{C}\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}\overline{B}\overline{C}D$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}\overline{B}C\overline{D}$	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}\overline{B}CD$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}B\overline{C}\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}B\overline{C}D$	1	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}BC\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}BCD$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$AB\overline{C}\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$AB\overline{C}D$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$ABC\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$ABCD$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}\overline{B}\overline{C}\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}\overline{B}\overline{C}D$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}\overline{B}C\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}\overline{B}CD$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0

$A'B'CDE'F'GH + A'BC'DE'F'H' = 00110100 + 0101000$

TRAFFIC LIGHT CONTROLLER

K MAP OUTPUT (NORTH-SOUTH GREEN)

A = NS Red D = EW Red G = Traffic on EW
B = NS Yellow E = EW Yellow H = Timer
C = NS Green F = EW Green

	$\overline{E}\overline{F}\overline{G}\overline{H}$	$\overline{E}\overline{F}\overline{G}H$	$\overline{E}\overline{F}G\overline{H}$	$\overline{E}\overline{F}GH$	$\overline{E}F\overline{G}\overline{H}$	$\overline{E}F\overline{G}H$	$\overline{E}FG\overline{H}$	$\overline{E}FGH$	$E\overline{F}\overline{G}\overline{H}$	$E\overline{F}\overline{G}H$	$EFG\overline{H}$	$EFGH$	$\overline{E}\overline{F}\overline{G}\overline{H}$	$\overline{E}\overline{F}\overline{G}H$	$\overline{E}\overline{F}G\overline{H}$	$\overline{E}\overline{F}GH$
$\overline{A}\overline{B}\overline{C}\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}\overline{B}\overline{C}D$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}\overline{B}C\overline{D}$	1	1	0	1	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}\overline{B}CD$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}B\overline{C}\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}B\overline{C}D$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}BC\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}BCD$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$A\overline{B}\overline{C}\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$A\overline{B}\overline{C}D$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$A\overline{B}C\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$A\overline{B}CD$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$AB\overline{C}\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	1	1	0
$AB\overline{C}D$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$ABC\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$ABCD$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0

$A'B'CDE'F'G' + AB'C'D'EF'H + A'B'CDE'F'GH' = 0011000 + 1000101 + 00110010$

TRAFFIC LIGHT CONTROLLER

K MAP OUTPUT (EAST-WEST RED)

A = NS Red D = EW Red G = Traffic on EW
B = NS Yellow E = EW Yellow H = Timer
C = NS Green F = EW Green

	$\overline{E}\overline{F}\overline{G}\overline{H}$	$\overline{E}\overline{F}\overline{G}H$	$\overline{E}\overline{F}G\overline{H}$	$\overline{E}\overline{F}GH$	$\overline{E}F\overline{G}\overline{H}$	$\overline{E}F\overline{G}H$	$\overline{E}FG\overline{H}$	$\overline{E}FGH$	$E\overline{F}\overline{G}\overline{H}$	$E\overline{F}\overline{G}H$	$EFG\overline{H}$	$EFGH$	$\overline{E}\overline{F}\overline{G}\overline{H}$	$\overline{E}\overline{F}\overline{G}H$	$\overline{E}\overline{F}G\overline{H}$	$\overline{E}\overline{F}GH$
$\overline{A}\overline{B}\overline{C}\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}\overline{B}\overline{C}D$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}\overline{B}\overline{C}D$	1	1	1	1	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}\overline{B}C\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}\overline{B}C\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}\overline{B}CD$	1	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}B\overline{C}\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}B\overline{C}D$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}BC\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}BC\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}BCD$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}BC\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}\overline{B}\overline{C}\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	1	1	0
$\overline{A}\overline{B}\overline{C}D$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}\overline{B}C\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}\overline{B}CD$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0

$A'B'CDE'F' + A'BC'DE'F'H' + AB'C'D'E'F'H = 001100 + 0101000 + 1000001$

K MAP OUTPUT (EAST-WEST YELLOW)

A = NS Red D = EW Red G = Traffic on EW
B = NS Yellow E = EW Yellow H = Timer
C = NS Green F = EW Green

	$\overline{E}\overline{F}\overline{G}\overline{H}$	$\overline{E}\overline{F}\overline{G}H$	$\overline{E}\overline{F}G\overline{H}$	$\overline{E}\overline{F}GH$	$\overline{E}F\overline{G}\overline{H}$	$\overline{E}F\overline{G}H$	$\overline{E}FG\overline{H}$	$\overline{E}FGH$	$E\overline{F}\overline{G}\overline{H}$	$E\overline{F}\overline{G}H$	$EFG\overline{H}$	$EFGH$	$\overline{E}\overline{F}\overline{G}\overline{H}$	$\overline{E}\overline{F}\overline{G}H$	$\overline{E}\overline{F}G\overline{H}$	$\overline{E}\overline{F}GH$
$\overline{A}\overline{B}\overline{C}\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}\overline{B}\overline{C}D$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}\overline{B}C\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}\overline{B}CD$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}B\overline{C}\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}B\overline{C}D$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}BC\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}BCD$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$A\overline{B}\overline{C}\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$A\overline{B}\overline{C}D$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$A\overline{B}C\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$A\overline{B}CD$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$AB\overline{C}\overline{D}$	0	0	0	0	0	1	1	0	0	0	0	0	1	0	0	1
$AB\overline{C}D$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$ABC\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$ABCD$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0

$AB'C'D'E'FH + AB'C'D'EF'H' = 1000011 + 1000100$

K MAP OUTPUT (EAST-WEST GREEN)

A = NS Red D = EW Red G = Traffic on EW
B = NS Yellow E = EW Yellow H = Timer
C = NS Green F = EW Green

	$\overline{E}\overline{F}\overline{G}\overline{H}$	$\overline{E}\overline{F}\overline{G}H$	$\overline{E}\overline{F}G\overline{H}$	$\overline{E}\overline{F}GH$	$\overline{E}F\overline{G}\overline{H}$	$\overline{E}F\overline{G}H$	$\overline{E}FG\overline{H}$	$\overline{E}FGH$	$E\overline{F}\overline{G}\overline{H}$	$E\overline{F}\overline{G}H$	$EFG\overline{H}$	$EFGH$	$\overline{E}\overline{F}\overline{G}\overline{H}$	$\overline{E}\overline{F}\overline{G}H$	$\overline{E}\overline{F}G\overline{H}$	$\overline{E}\overline{F}GH$
$\overline{A}\overline{B}\overline{C}\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}\overline{B}\overline{C}D$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}\overline{B}C\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}\overline{B}CD$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}B\overline{C}\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}B\overline{C}D$	0	1	1	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}BC\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$\overline{A}BCD$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$AB\overline{C}\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$AB\overline{C}D$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$ABC\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$ABCD$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$A\overline{B}\overline{C}\overline{D}$	0	0	0	0	1	0	0	1	0	0	0	0	0	0	0	0
$A\overline{B}\overline{C}D$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$A\overline{B}C\overline{D}$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$A\overline{B}CD$	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0

$A'BC'DE'F'H + AB'C'D'E'FH' = 0101000 + 1000010$

STATE DIAGRAM



TRAFFIC LIGHT CONTROLLER

MODULE

```
`timescale 1ns / 1ps

/*
    Group Members: Kevin Ingram and Warren Seto

    Lab Name: Traffic Light Controller (Lab 3)
    Project Name: eng312_proj3
    Design Name: Traffic_eng312_proj3.v
    Design Description: Verilog Module to Implement
*/

module Traffic
(
    input [4:0] nsCounter,
    input [3:0] ewCounter,
    input [1:0] yellowCounter,
    input NS_VEHICLE_DETECT,
    input EW_VEHICLE_DETECT,
    output reg NS_RED,
    output reg NS_YELLOW,
    output reg NS_GREEN,
    output reg EW_RED,
    output reg EW_YELLOW,
    output reg EW_GREEN
);

    begin
        NS_RED <= 0;
        NS_YELLOW <= 0;
        NS_GREEN <= 1;
        EW_RED <= 1;
        EW_YELLOW <= 0;
        EW_GREEN <= 0;
    end


end
```

001100


S1



MODULE

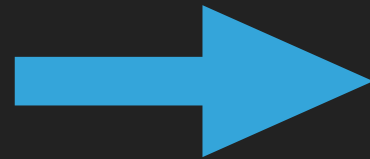
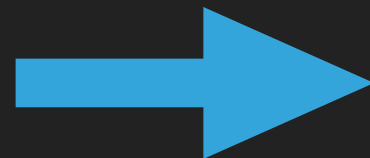
```
always @ (nsCounter) begin
    if (nsCounter == 31 & EW_VEHICLE_DETECT &
NS_GREEN) begin
        NS_RED <= 0;
        NS_YELLOW <= 1;
        NS_GREEN <= 0;
        EW_RED <= 1;
        EW_YELLOW <= 0;
        EW_GREEN <= 0;
    end
end
```




```
always @ (ewCounter) begin
    if (ewCounter == 15 & EW_GREEN) begin
        NS_RED <= 1;
        NS_YELLOW <= 0;
        NS_GREEN <= 0;
        EW_RED <= 0;
        EW_YELLOW <= 1;
        EW_GREEN <= 0;
    end
end
```

MODULE


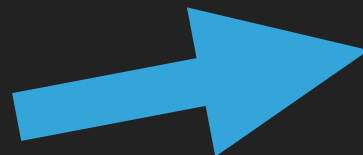
```
always @ (yellowCounter) begin
    if (yellowCounter == 3 & NS_YELLOW) begin
        NS_RED <= 1;
        NS_YELLOW <= 0;
        NS_GREEN <= 0;
        EW_RED <= 0;
        EW_YELLOW <= 0;
        EW_GREEN <= 1;
    end
end
```



```
    if (yellowCounter == 3 & EW_YELLOW) begin
        NS_RED <= 0;
        NS_YELLOW <= 0;
        NS_GREEN <= 1;
        EW_RED <= 1;
        EW_YELLOW <= 0;
        EW_GREEN <= 0;
    end
end
endmodule
```


TRAFFIC LIGHT CONTROLLER

TESTS

```
`timescale 1ns / 1ps

/*
    Group Members: Kevin Ingram and Warren Seto

    Lab Name: Traffic Light Controller (Lab 3)
    Project Name: eng312_proj3
    Design Name: Traffic_Test_A_eng312_proj3.v
    Design Description: Verilog Test Bench to Implement Test A (3 AM)
*/

module Traffic_Test;

    // Inputs
    reg NS_VEHICLE_DETECT;
    reg EW_VEHICLE_DETECT;

    // Outputs
    wire NS_RED;
    wire NS_YELLOW;
    wire NS_GREEN;
    wire EW_RED;
    wire EW_YELLOW;
    wire EW_GREEN;

    // Clock
    reg clk;

    // Counters
    wire[4:0] count1;
    wire[3:0] count2;
    wire[1:0] count3;

    // Counter Modules
    nsCounter clock1(clk, count1);      // Count a total of 32 seconds
    ewCounter clock2(clk, count2);      // Counts a total of 16 seconds
    yellowCounter clock3(clk, count3);  // Counts a total of 4 seconds

    // Main Traffic Module
    Traffic CORE (count1, count2, count3, NS_VEHICLE_DETECT, EW_VEHICLE_DETECT, NS_RED, NS_YELLOW,
    NS_GREEN, EW_RED, EW_YELLOW, EW_GREEN);
```

TRAFFIC LIGHT CONTROLLER


TEST A (3 AM)

```
initial begin
    clk = 0;
    NS_VEHICLE_DETECT = 0;
    EW_VEHICLE_DETECT = 0;

    $display("          NS | EW ");
    $display("        R Y G R Y G ");

    #1000 $finish;
end

always begin
    #1 clk = ~clk;
end
```

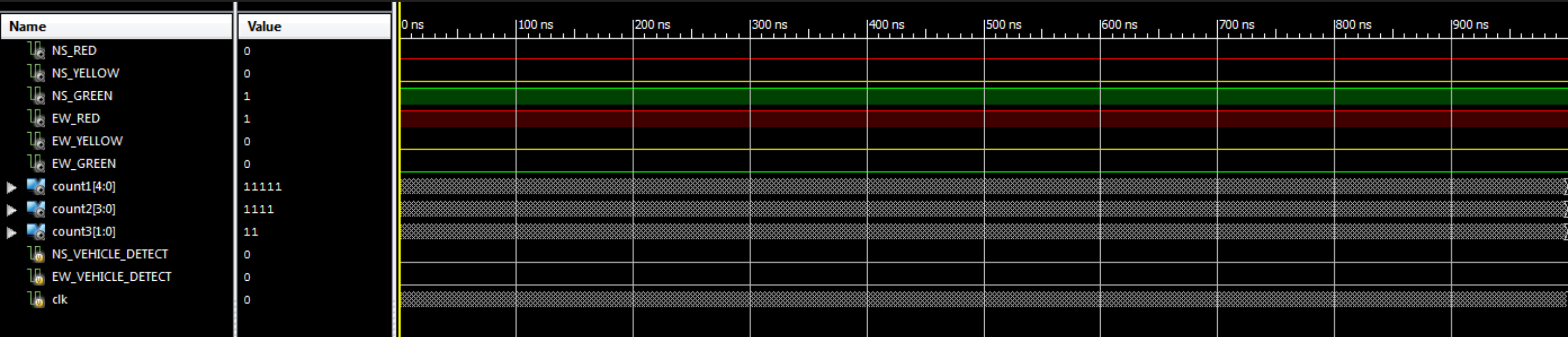

TRAFFIC LIGHT CONTROLLER

TEST B (6 AM)


```
initial begin
    clk = 0;
    NS_VEHICLE_DETECT = 0;
    EW_VEHICLE_DETECT = 1;

    $display("          NS | EW ");
    $display("          R Y G R Y G ");

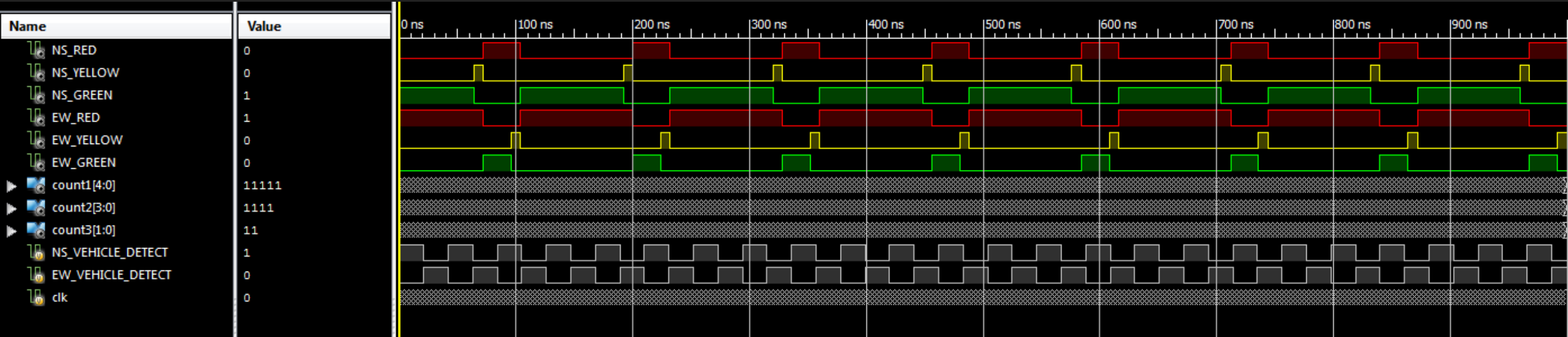    #1000 $finish;
end

always begin
    #1 clk = ~clk;
end

always @ (clk) begin
    if ($time % 21 == 0) begin
        NS_VEHICLE_DETECT = ~NS_VEHICLE_DETECT;
        EW_VEHICLE_DETECT = ~EW_VEHICLE_DETECT;
    end
end
```



TRAFFIC LIGHT CONTROLLER

TEST C (9 AM)

```
initial begin
    clk = 0;
    NS_VEHICLE_DETECT = 0;
    EW_VEHICLE_DETECT = 1;


    $display("          NS | EW ");
    $display("          R Y G R Y G ");

    #1000 $finish;
end

always begin
    #1 clk = ~clk;
end

always @ (clk) begin
    if ($time % 15 == 0) begin
        NS_VEHICLE_DETECT = ~NS_VEHICLE_DETECT;
    end

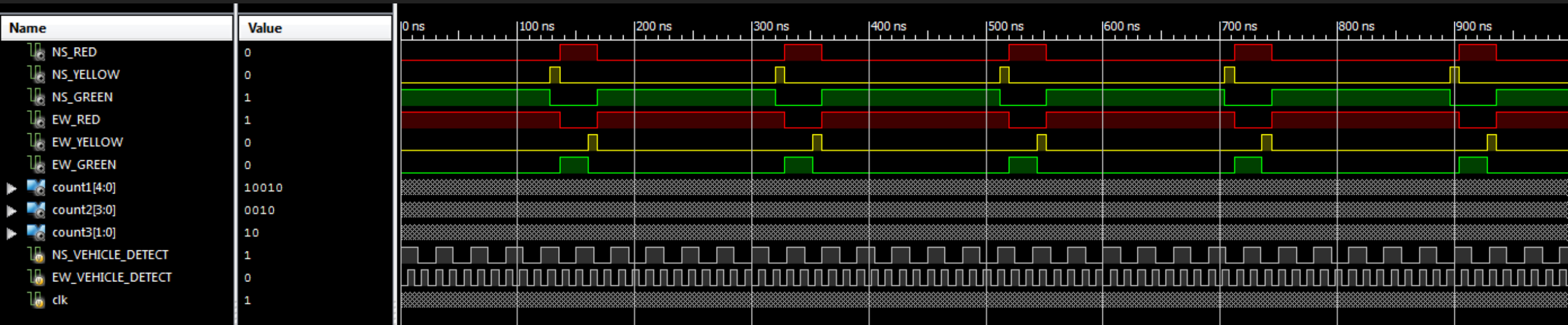    if ($time % 6 == 0) begin
        EW_VEHICLE_DETECT = ~EW_VEHICLE_DETECT;
    end
end
```



TRAFFIC LIGHT CONTROLLER

TEST D (11 AM)

```
initial begin
    clk = 0;
    NS_VEHICLE_DETECT = 0;
    EW_VEHICLE_DETECT = 1;


    $display("          NS | EW ");
    $display("          R Y G R Y G ");

    #1000 $finish;
end

always begin
    #1 clk = ~clk;
end

always @ (clk) begin
    if ($time % 6 == 0) begin
        NS_VEHICLE_DETECT = ~NS_VEHICLE_DETECT;
    end

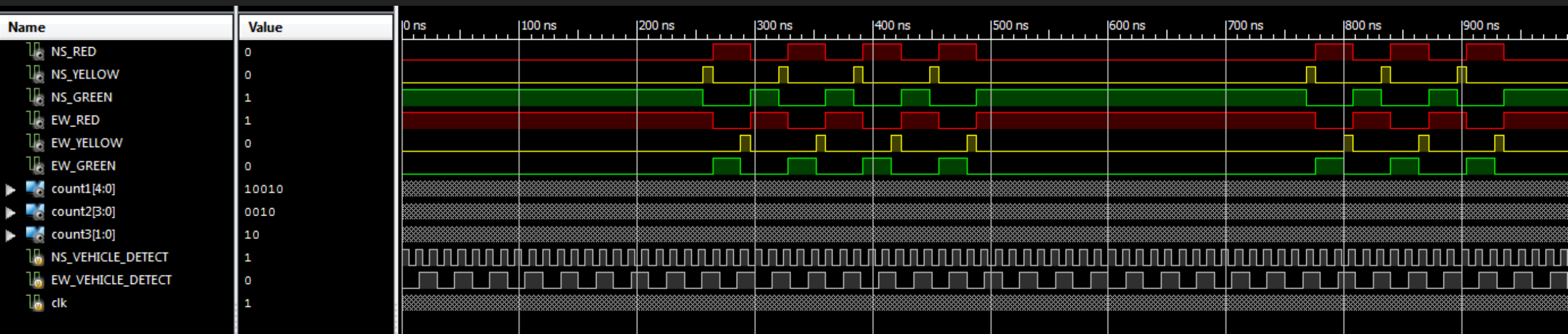    if ($time % 15 == 0) begin
        EW_VEHICLE_DETECT = ~EW_VEHICLE_DETECT;
    end
end
```



TRAFFIC LIGHT CONTROLLER

TEST E (1 PM)

```
initial begin
    clk = 0;
    NS_VEHICLE_DETECT = 0;
    EW_VEHICLE_DETECT = 1;


    $display("          NS | EW ");
    $display("          R Y G R Y G ");

    #1000 $finish;
end

always begin
    #1 clk = ~clk;
end

always @ (clk) begin
    if ($time % 2 == 0) begin
        NS_VEHICLE_DETECT = ~NS_VEHICLE_DETECT;
    end

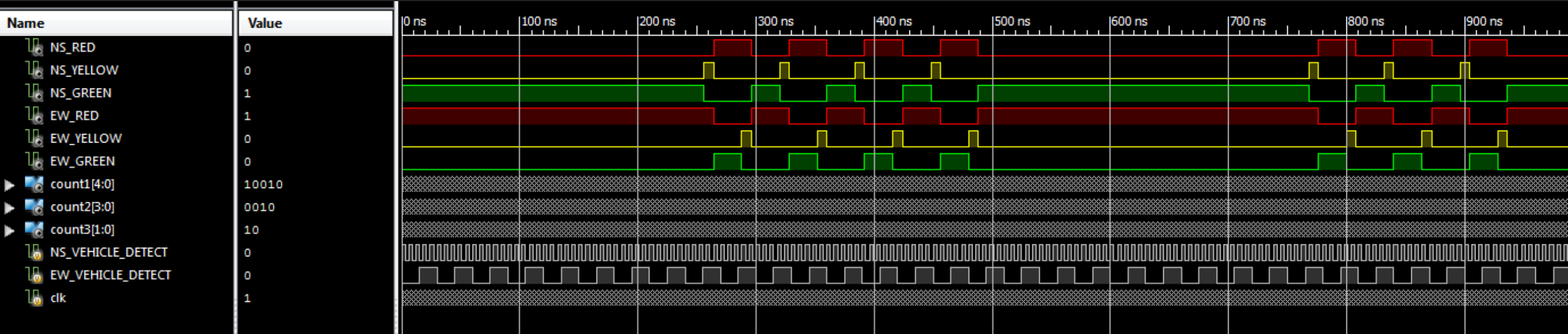    if ($time % 15 == 0) begin
        EW_VEHICLE_DETECT = ~EW_VEHICLE_DETECT;
    end
end
```



TRAFFIC LIGHT CONTROLLER

TEST F (2 PM)

```
initial begin
    clk = 0;
    NS_VEHICLE_DETECT = 0;
    EW_VEHICLE_DETECT = 1;


    $display("          NS | EW ");
    $display("          R Y G R Y G ");

    #1000 $finish;
end

always begin
    #1 clk = ~clk;
end

always @ (clk) begin
    if ($time % 15 == 0) begin
        NS_VEHICLE_DETECT = ~NS_VEHICLE_DETECT;
    end

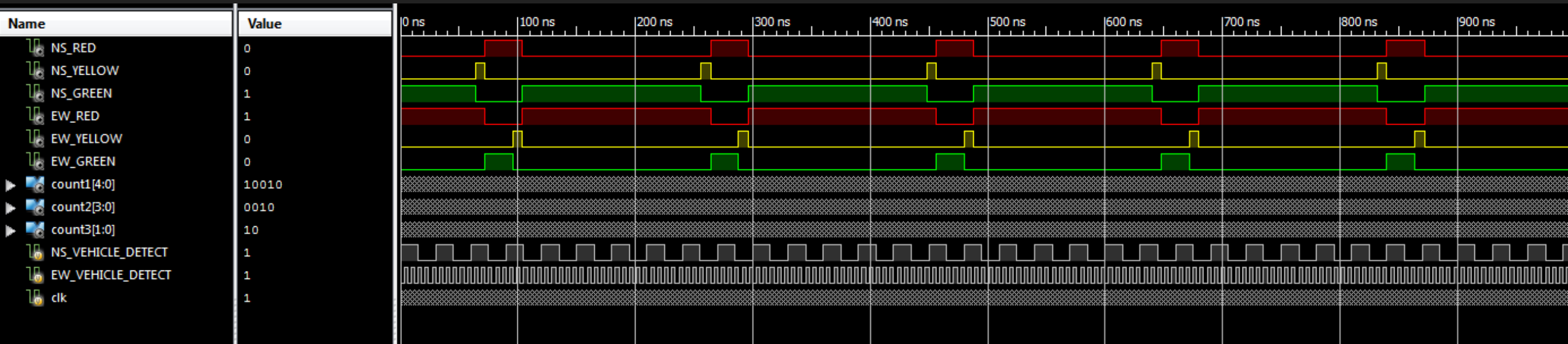    if ($time % 2 == 0) begin
        EW_VEHICLE_DETECT = ~EW_VEHICLE_DETECT;
    end
end
```



TRAFFIC LIGHT CONTROLLER

TEST G (3 PM)

```
initial begin
    clk = 0;
    NS_VEHICLE_DETECT = 0;
    EW_VEHICLE_DETECT = 1;


    $display("          NS | EW ");
    $display("          R Y G R Y G ");

    #1000 $finish;
end

always begin
    #1 clk = ~clk;
end

always @ (clk) begin
    if ($time % 2 == 0) begin
        NS_VEHICLE_DETECT = ~NS_VEHICLE_DETECT;
    end

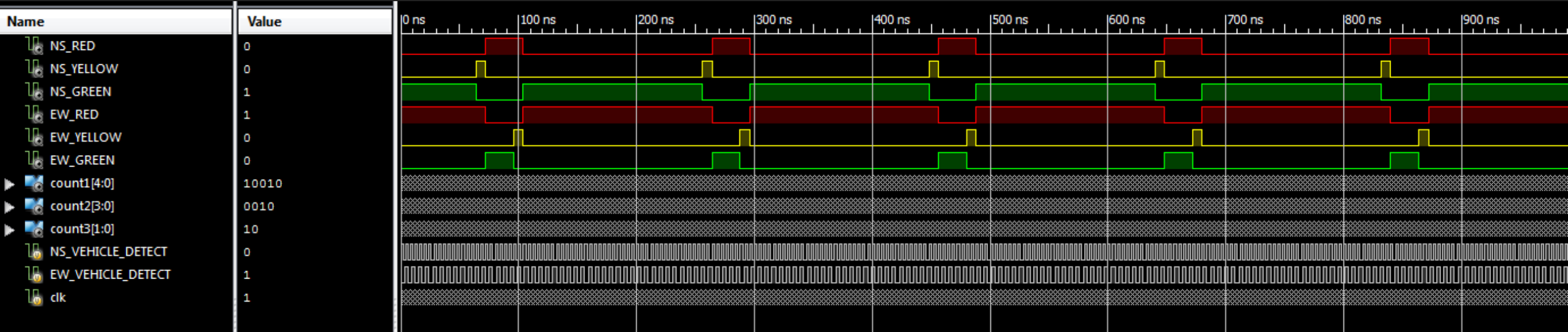    if ($time % 3 == 0) begin
        EW_VEHICLE_DETECT = ~EW_VEHICLE_DETECT;
    end
end
```



TRAFFIC LIGHT CONTROLLER


TEST H (RUSH HOUR)

```
initial begin
    clk = 0;
    NS_VEHICLE_DETECT = 1;
    EW_VEHICLE_DETECT = 1;

    $display("          NS | EW ");
    $display("R Y G R Y G ");

    #1000 $finish;
end

always begin
    #1 clk = ~clk;
end
```

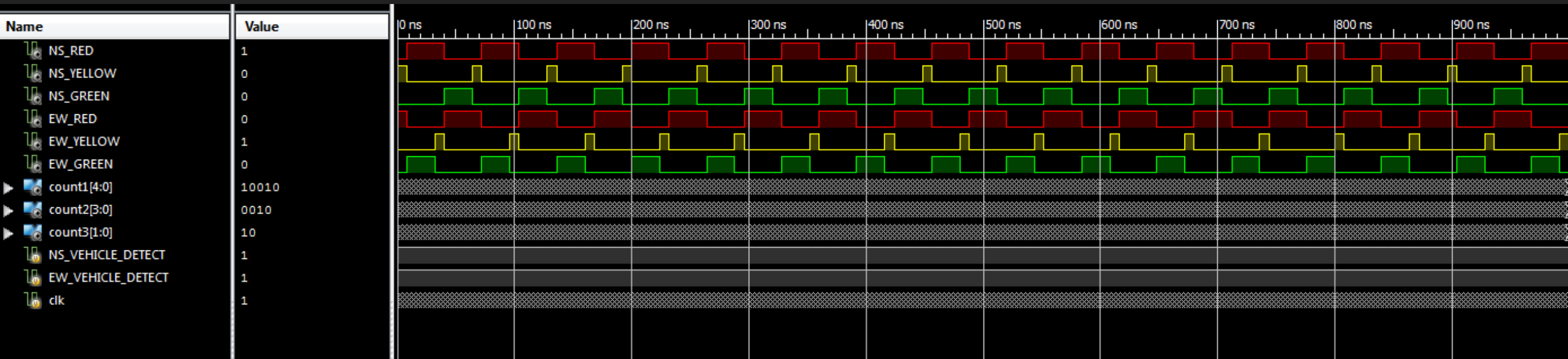



TRAFFIC LIGHT CONTROLLER

Kevin Ingram
Warren Seto